

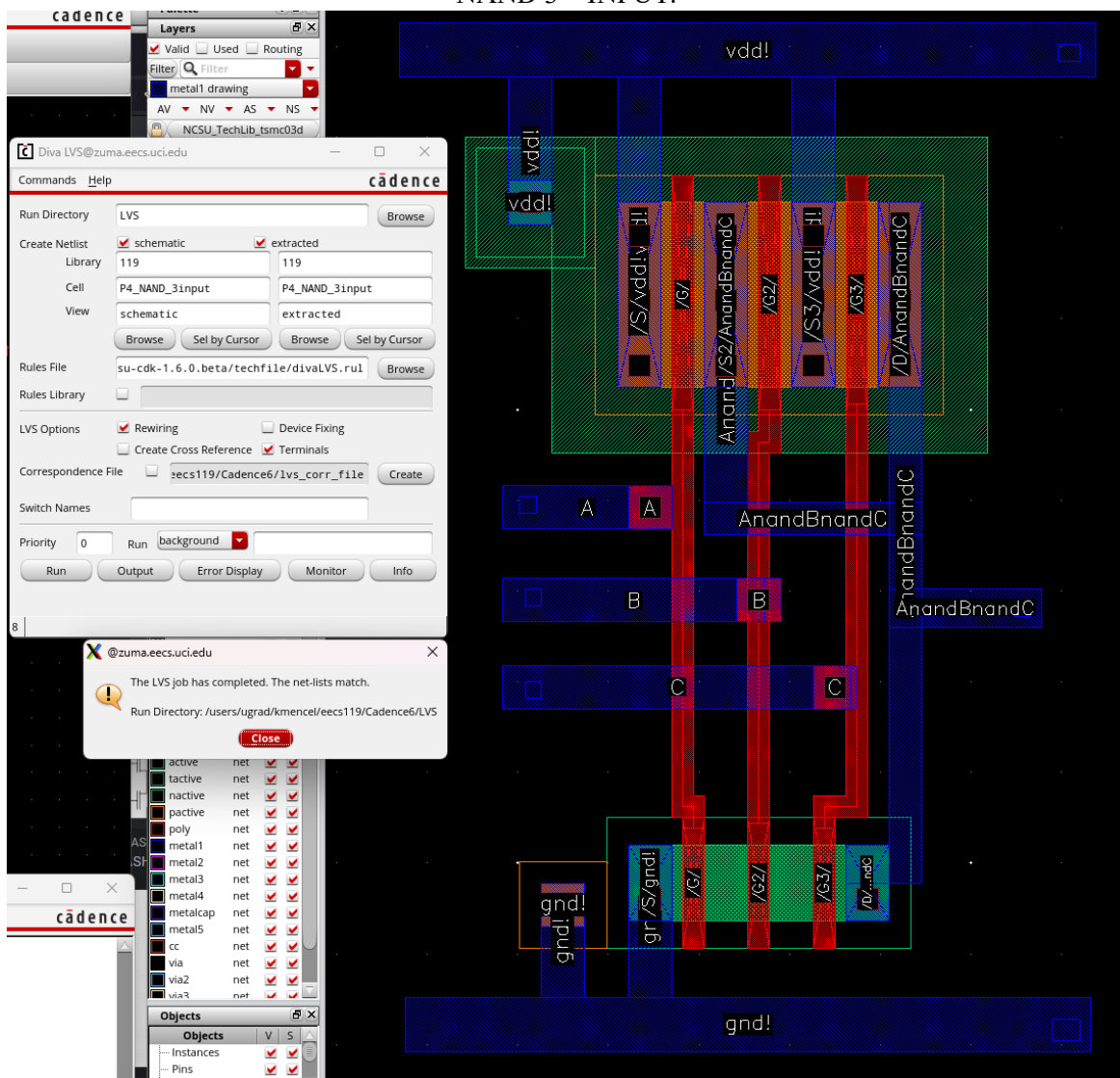


NAND 3 – INPUT:

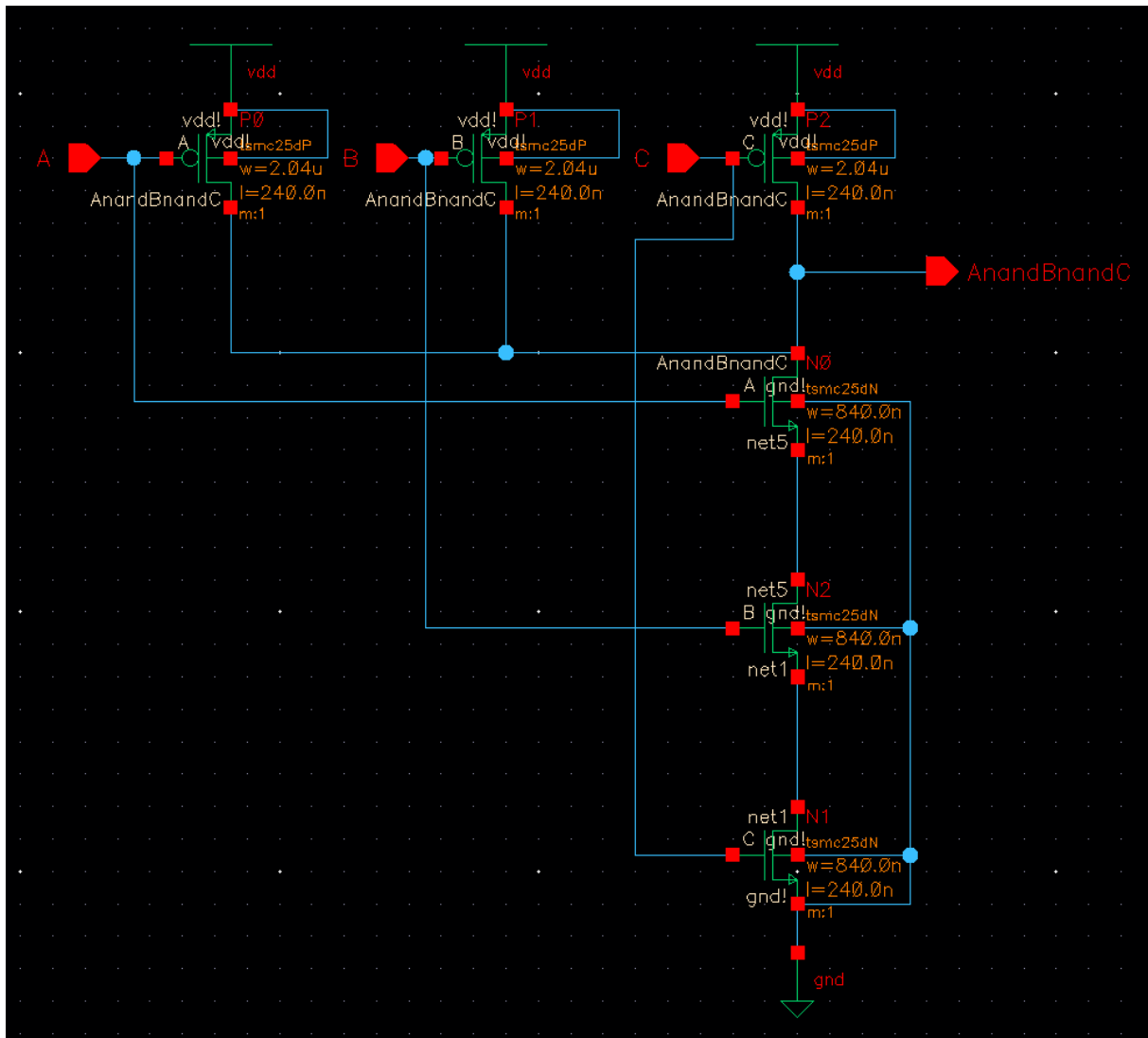

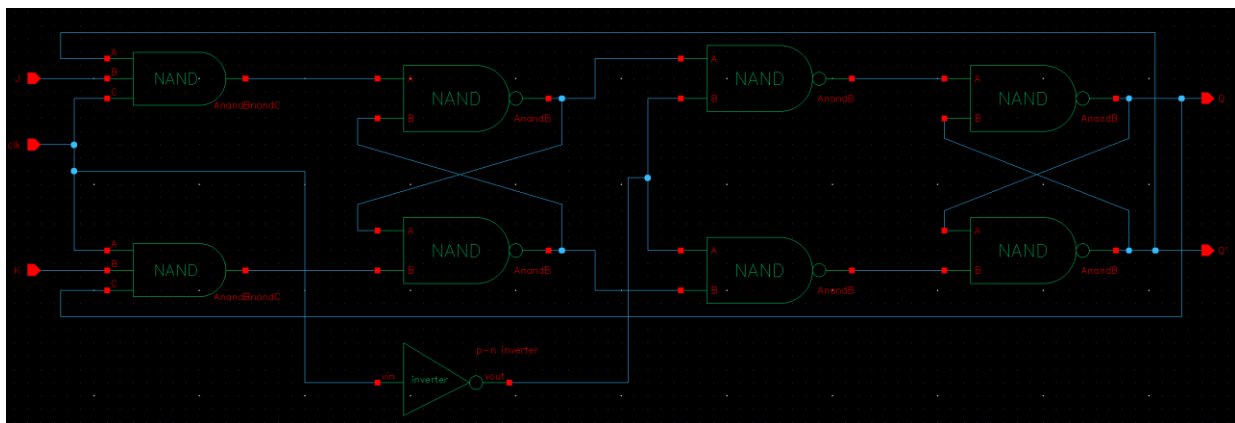




JK master slave flip flop



Transient Response


Wed Nov 22 01:17:12 2023

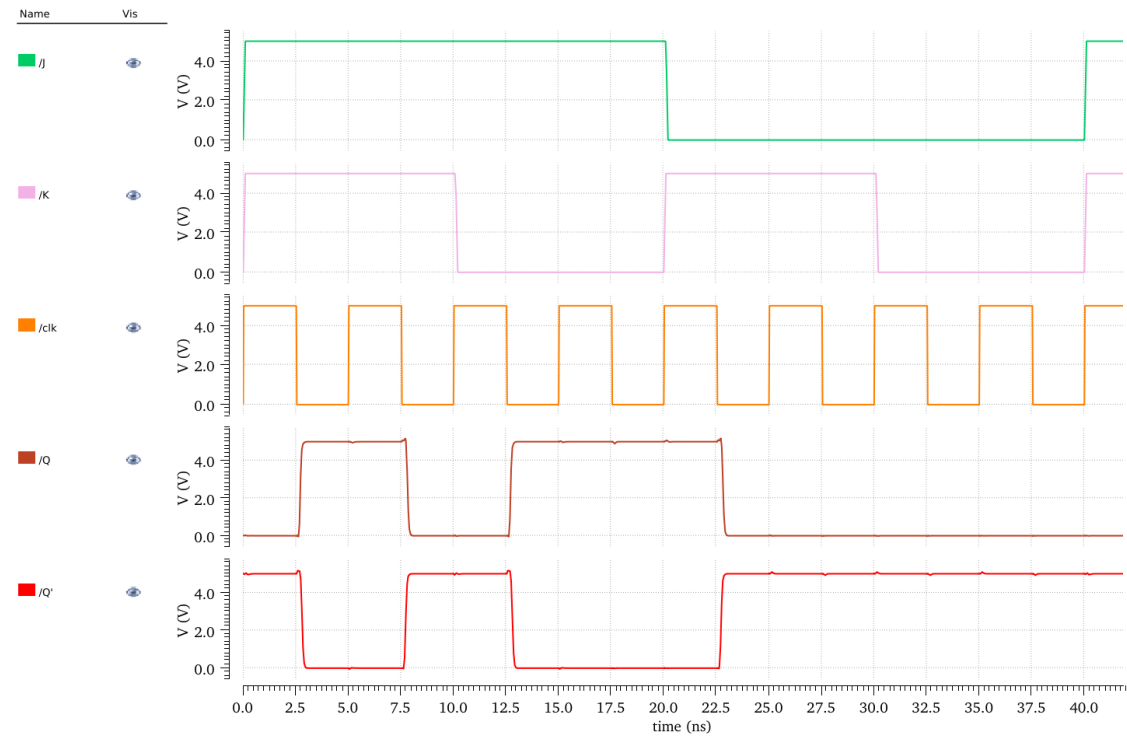

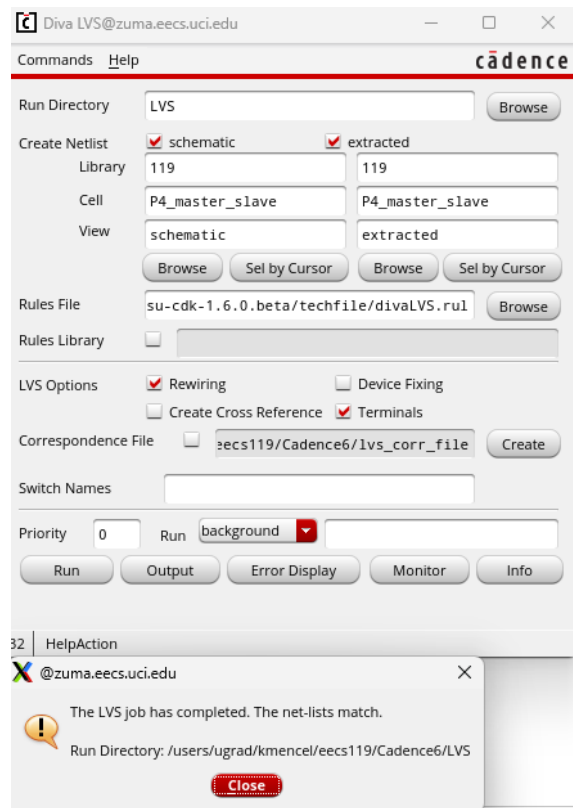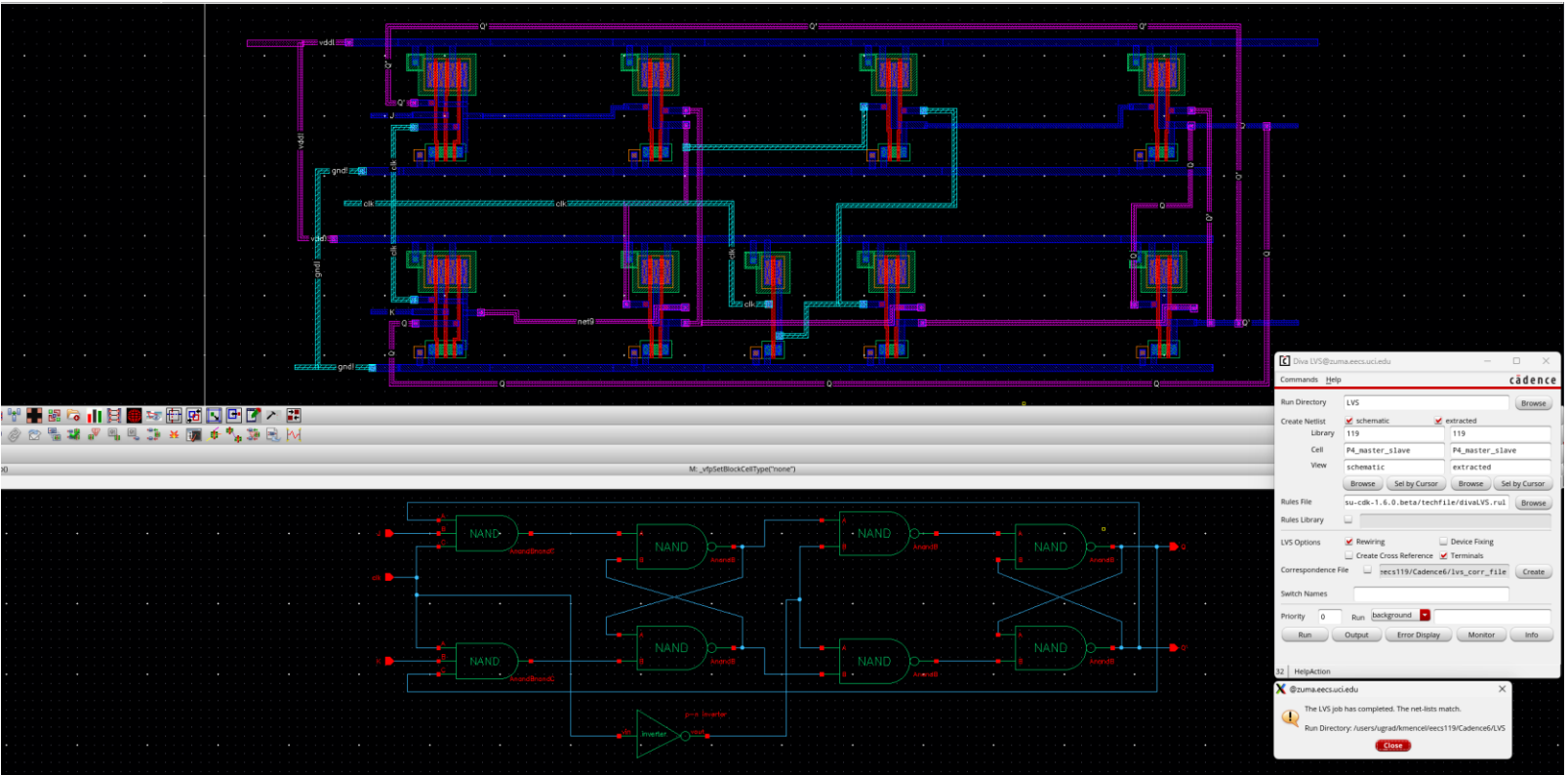



LVS check

Parasitic capacitance:

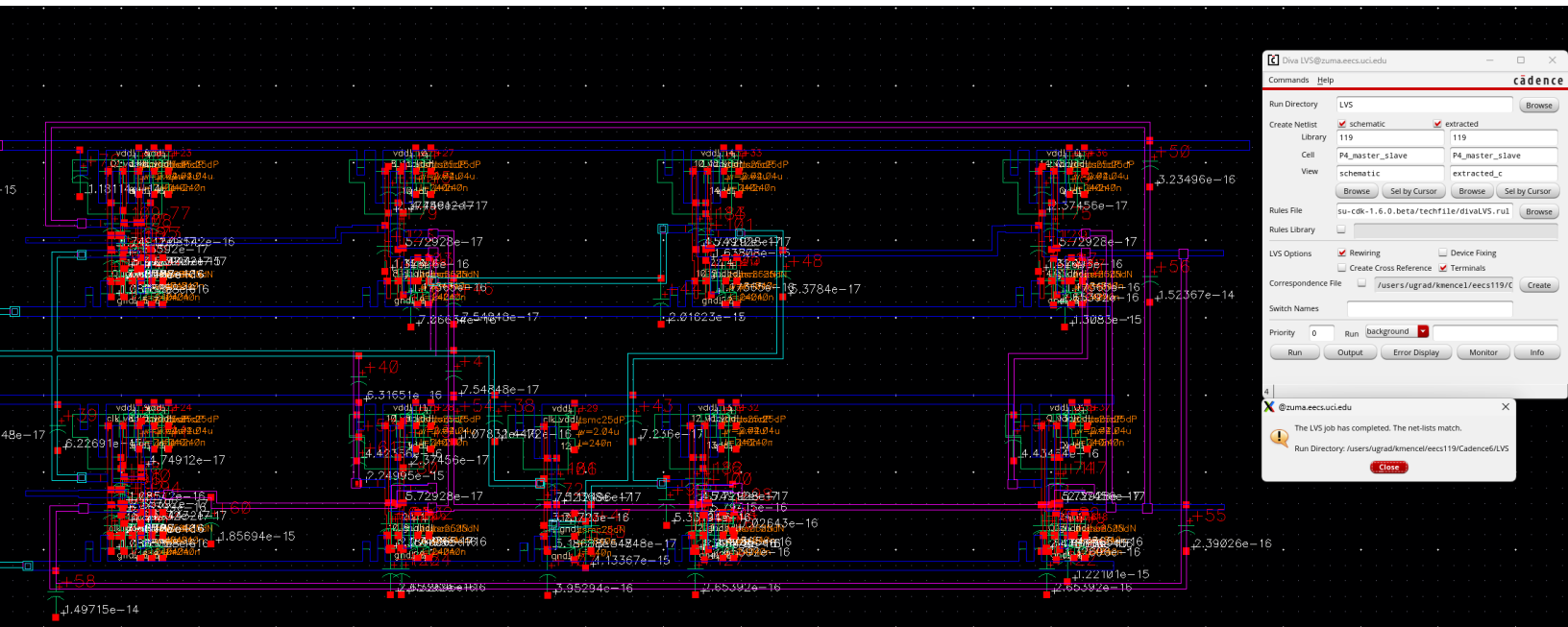


4 bit counter

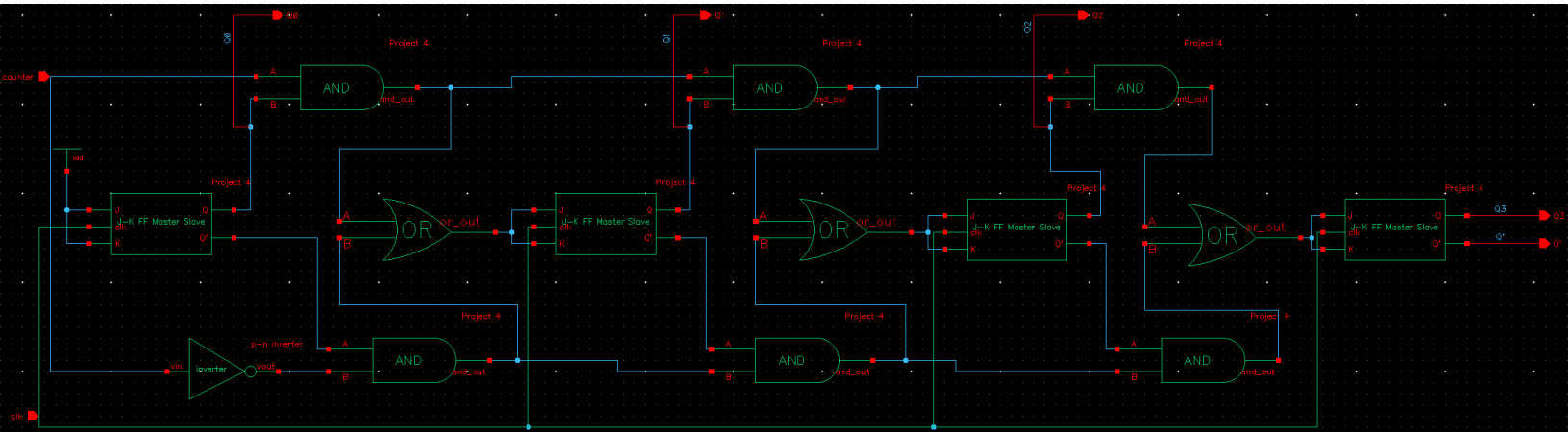

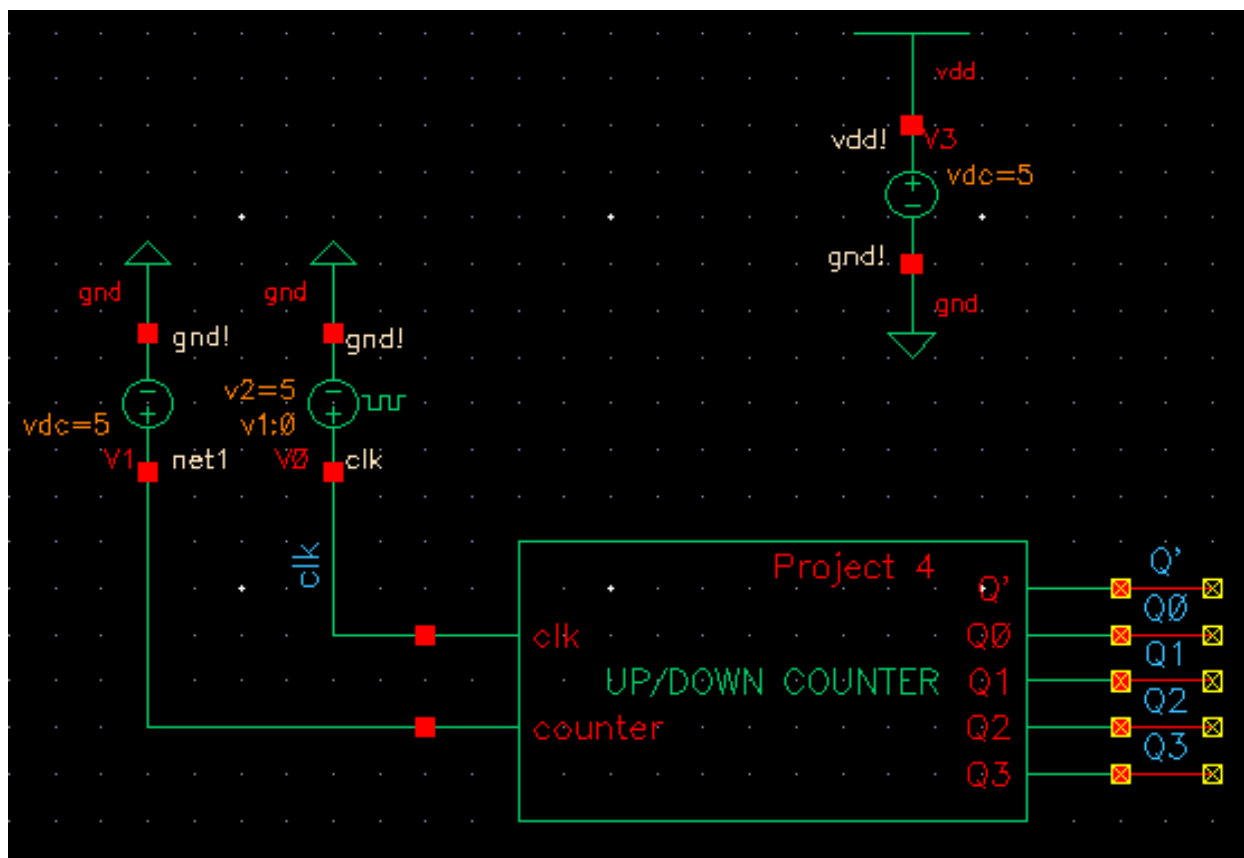


Transient Response

Wed Nov 22 01:53:15 2023

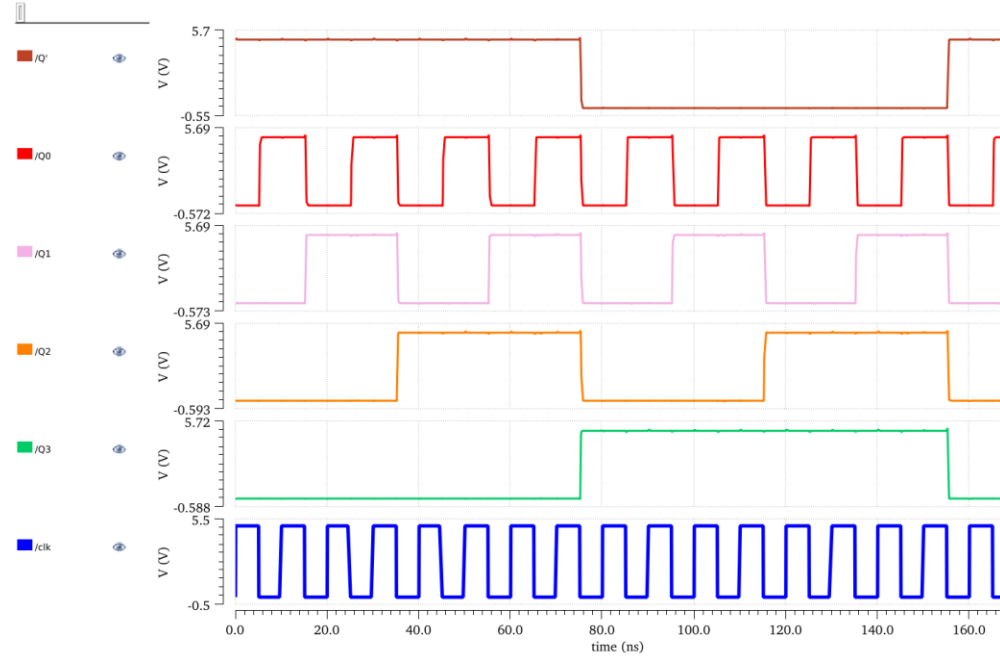

Transient Response

Wed Nov 22 02:03:50 2023

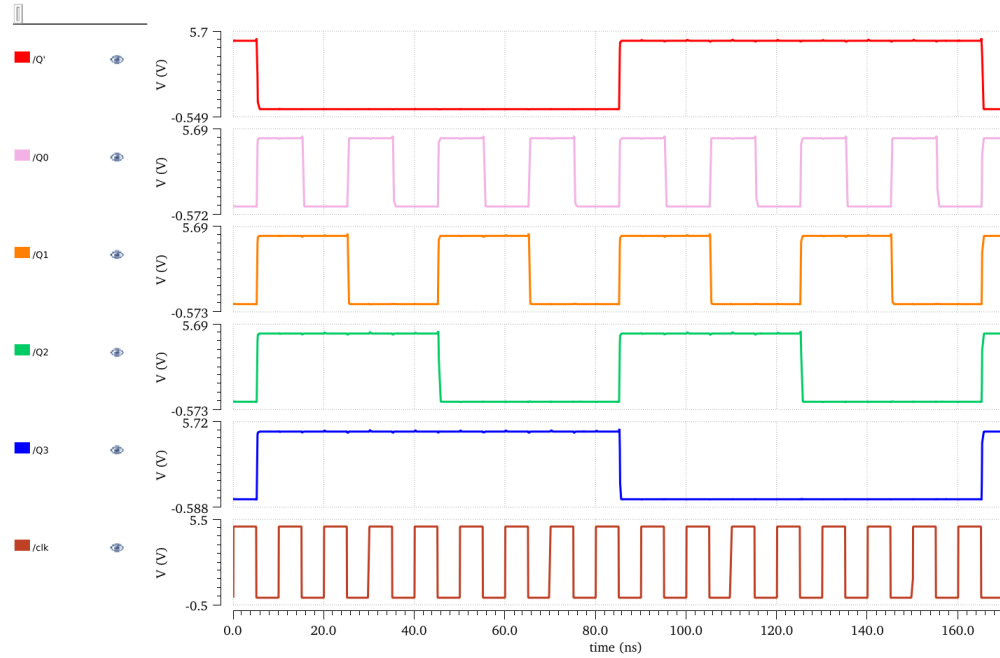

Layout

